









## CHAPTER 9: ELECTRONICS



### QUIZ

Any gate can be built from NAND or NOR gates. For example, NAND gates can be combined in the following circuits to create a NOT, an AND and an OR gate.

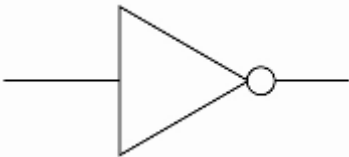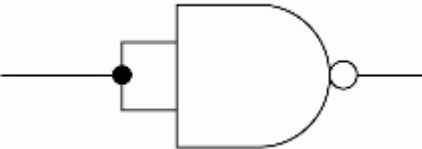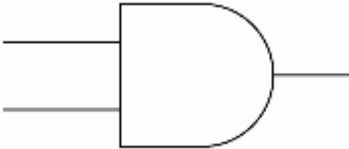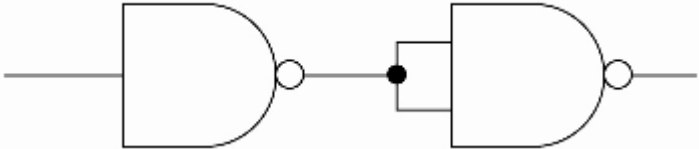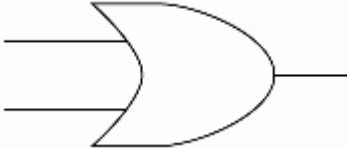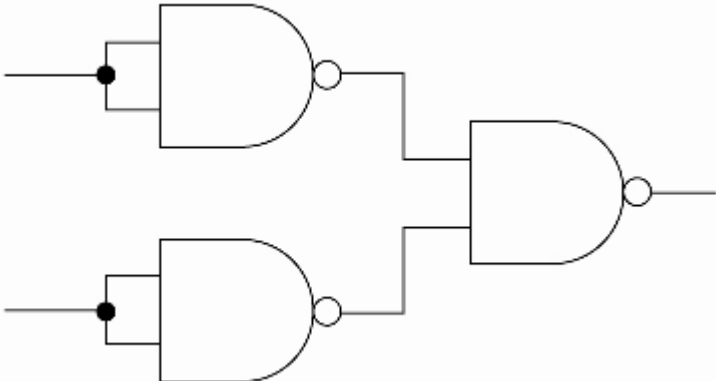	Gate	Combination of NAND gates
NOT		
AND		
OR		

Try to draw the NAND gate combination to create a NOR gate!