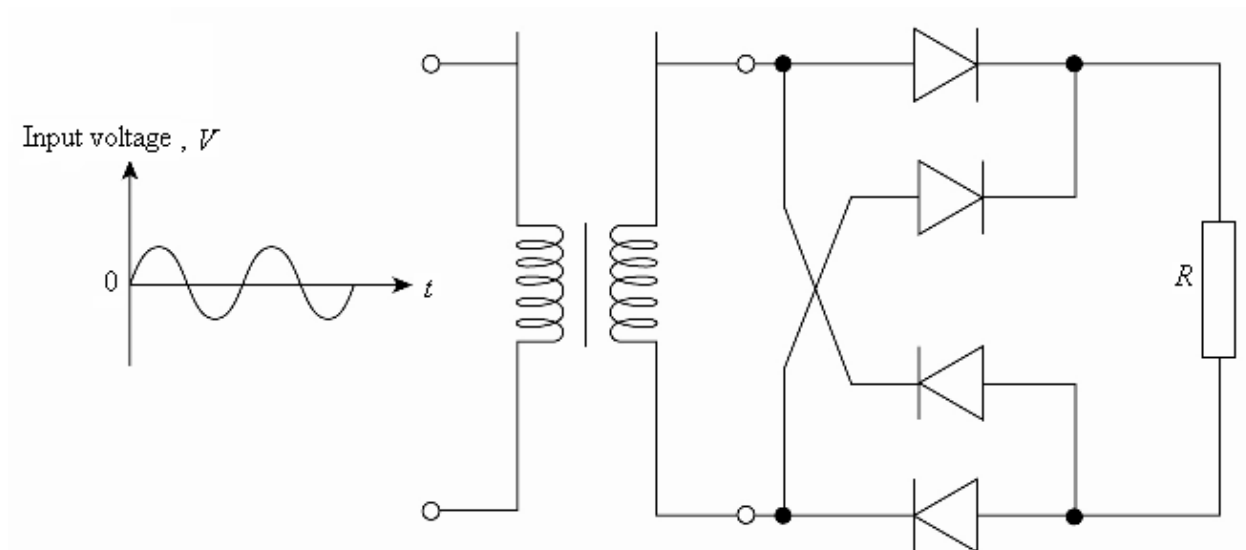


CHAPTER 9: ELECTRONICS

EXTRA QUESTION



With four diodes arranged in a rectification circuit as shown, can you draw the output voltage, V_R , on the graph given?

Output voltage: *Output voltage, V_R*

